



Pre-Health Post-Baccalaureate Program  
PHY2054 Study Guide & Practice Problems

Date:

10 / 12 - 10 / 16

Topics Covered:

Capacitors  
RC Circuits

Created by Isaac Loy




# Capacitors

- A capacitor refers to a pair of conductors separated by an insulated layer
- Capacitors charge when attached to a battery, therefore increasing the potential difference until reaching the point  $\Delta V_c = \mathcal{E}$
- At this point of full charge, the charge on each plate of the capacitor is  $Q = C \Delta V$
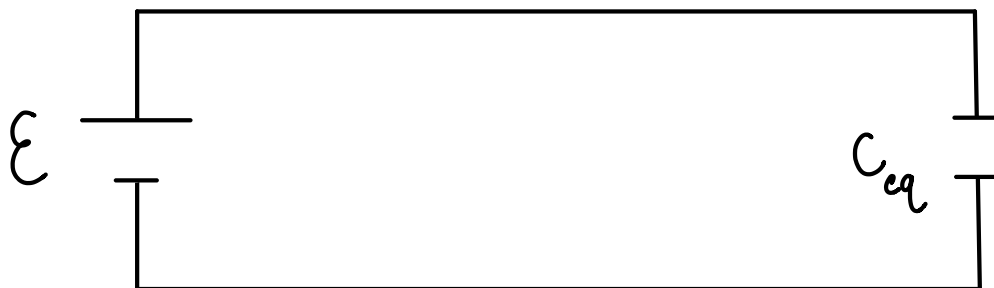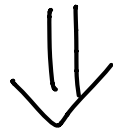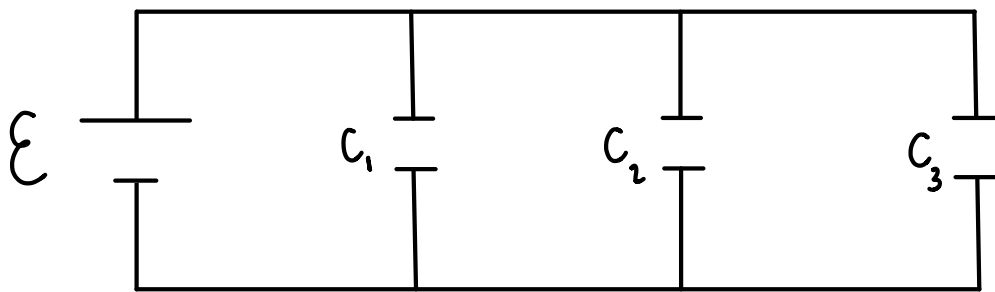
# Capacitors in Parallel

- When thinking about equivalent capacitance, we are going to do the opposite of what we did to find equivalent resistance
- For capacitors in parallel, the equivalent capacitance equals the sum of the individual capacitors:


$$C_{eq\ par.} = C_1 + C_2 + C_3 + \dots + C_N$$


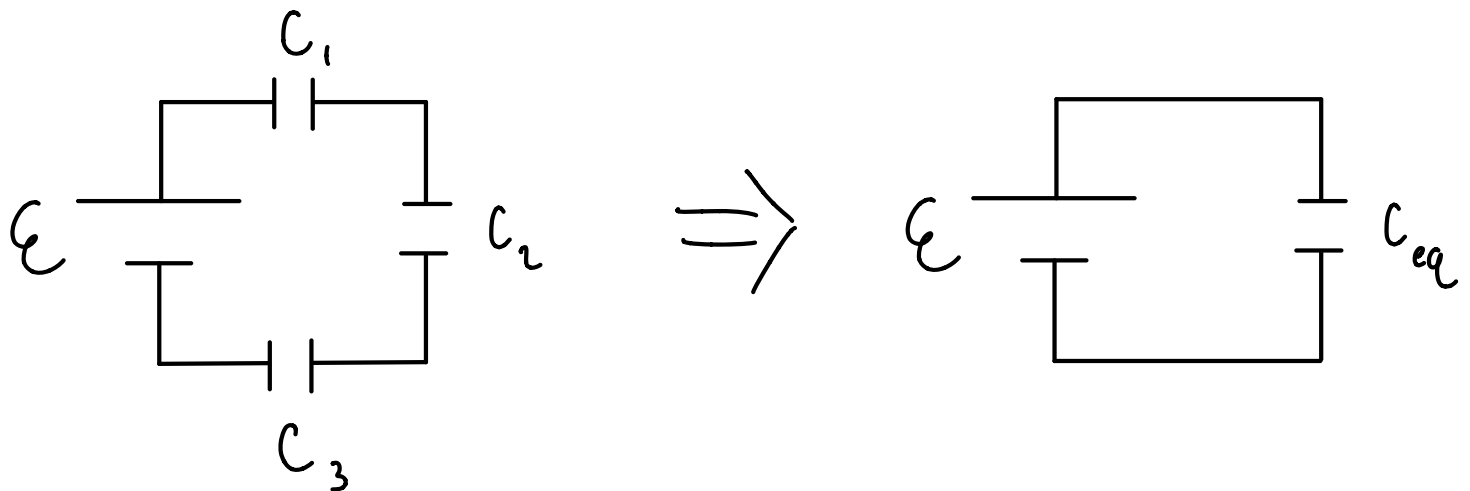
# Capacitors in Series



- For capacitors in series, the equivalent capacitance equals the inverse of the sum of the inverse of the individual capacitors (was that confusing? I confused myself just writing it. If so, see the below formula).

$$C_{eq_{ser.}} = \left( \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_n} \right)^{-1}$$


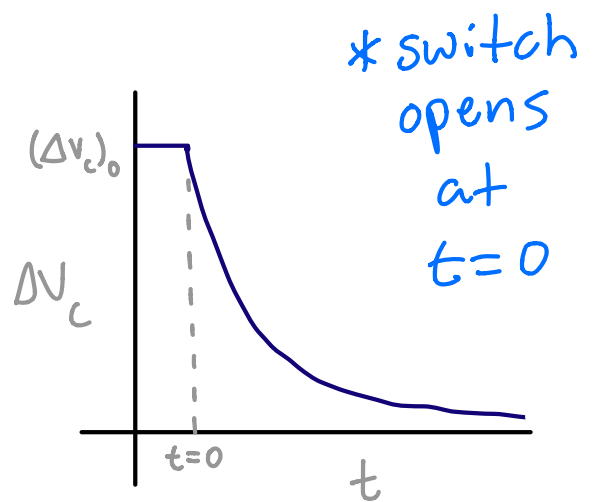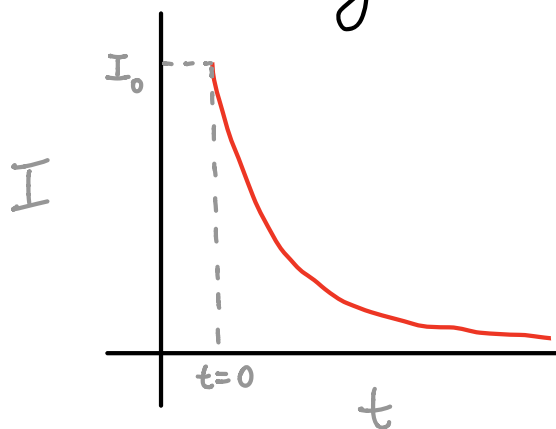
# RC Currents

- We have dealt with circuits in which the current is constant... but what if the current changes with respect to time due to a charging or discharging capacitor?
- Starting with a fully **charged capacitor**, the initial current (driven by the capacitor) and the capacitor voltage (separation of charge) begin high, and exponentially decrease over time as the capacitor discharges



— Current and voltage in a discharging RC circuit are mathematically modeled as:

$$I = I_0 e^{-\frac{t}{RC}}$$

$$\Delta V_c = (\Delta V_c)_0 e^{-\frac{t}{RC}}$$

Where :



$t \rightarrow$  time (s)

$R \rightarrow$  resistance ( $\Omega$ )

$C \rightarrow$  capacitance (F)

— On the other hand, if we have a discharged capacitor, our dynamic slightly changes:

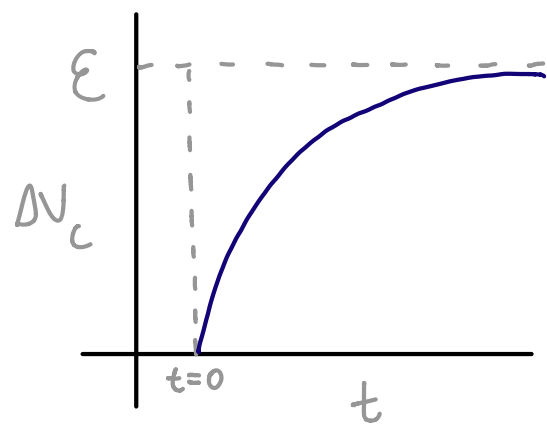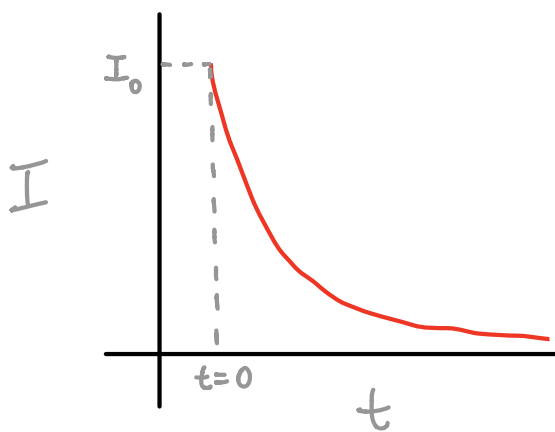- The battery's potential difference increases over time while charging.
- The potential difference opposes the current, so the current decreases over time.



\* switch closes at  $t=0$

— Current and voltage in a charging RC circuit are mathematically modeled as:

$$I = I_0 e^{-\frac{t}{RC}}$$

$$\Delta V_c = \mathcal{E} \left( 1 - e^{-\frac{t}{RC}} \right)$$